

Question number	Answer	Additional guidance	Mark
3(a)	<ul style="list-style-type: none"> connect ammeter in series (with thermistor) (1) connect voltmeter in parallel (with thermistor) (1) reverse (connections for) one of the cells (1) 	allow idea that meters should be swapped for two marks (equivalent to first two points)	(3)

Question number	Answer	Additional guidance	Mark
3(b)(i)	<p>Any one of the following reasons:</p> <ul style="list-style-type: none"> the thermistor and the water are at the same temperature (1) large volume of water gives a steady temperature rise (1) 	<p>accept idea that only small part of thermometer would be in contact with a thermistor in air</p> <p>accept difficult to control change in temperature of thermistor when heated in air</p>	(1)

Question number	Answer	Additional guidance	Mark
3(b)(ii)	<p>Any one of the following developments to the procedure:</p> <ul style="list-style-type: none"> add ice to increase lower limit of temperature range (1) use liquid with higher boiling point to increase upper limit of temperature range (1) 	accept named liquid with higher boiling point, e.g. oil	(1)

Question number	Answer	Additional guidance	Mark
3(c)(i)	<p>A comparison and contrast that must include at least one similarity and one difference from the following points to a maximum of three marks:</p> <p>Similarities</p> <ul style="list-style-type: none"> resistance of both changes with temperature (1) both graphs show a non-linear relationship (1) data comparison, e.g. both have the same resistance at 80°C (1) 		(3)

	<p>Differences</p> <ul style="list-style-type: none"> resistance of A decreases with temperature but resistance of B increases with temperature (1) for A, (largest slope/rate of change) is at lower temperature but for B, (largest slope/rate of change) is at higher temperature(s) (1) for B, resistance is constant below 50°C but for A resistance is roughly constant above 60°C (1) 	accept (smallest slope/rate of change) for A is at higher temperature but (smallest slope/rate of change) for B is at lower temperature	
--	---	---	--

Question number	Answer	Mark
3(c)(ii)	B	(1)

Question number	Answer	Mark
4(a)(i)	The earth wire discharges the aircraft to prevent sparking which could ignite the fuel/cause a fire	(1)

Question number	Answer	Additional guidance	Mark
4(a)(ii)	<p>An explanation that combines identification – understanding (1 mark) and reasoning/justification – understanding (1 mark):</p> <ul style="list-style-type: none"> friction between aircraft and air (1) causes electron transfer between aircraft and air (1) 	<p>accept idea of air rubbing against wings ignore 'charge' and 'static'</p> <p>do not allow (for second mark) idea of protons moving</p>	(2)

Question number	Answer	Additional guidance	Mark
3(a)	<ul style="list-style-type: none"> connect ammeter in series (with thermistor) (1) connect voltmeter in parallel (with thermistor) (1) reverse (connections for) one of the cells (1) 	allow idea that meters should be swapped for two marks (equivalent to first two points)	(3)

Question number	Answer	Additional guidance	Mark
3(b)(i)	<p>Any one of the following reasons:</p> <ul style="list-style-type: none"> the thermistor and the water are at the same temperature (1) large volume of water gives a steady temperature rise (1) 	<p>accept idea that only small part of thermometer would be in contact with a thermistor in air</p> <p>accept difficult to control change in temperature of thermistor when heated in air</p>	(1)

Question number	Answer	Additional guidance	Mark
3(b)(ii)	<p>Any one of the following developments to the procedure:</p> <ul style="list-style-type: none"> add ice to increase lower limit of temperature range (1) use liquid with higher boiling point to increase upper limit of temperature range (1) 	accept named liquid with higher boiling point, e.g. oil	(1)

Question number	Answer	Additional guidance	Mark
3(c)(i)	<p>A comparison and contrast that must include at least one similarity and one difference from the following points to a maximum of three marks:</p> <p>Similarities</p> <ul style="list-style-type: none"> resistance of both changes with temperature (1) both graphs show a non-linear relationship (1) data comparison, e.g. both have the same resistance at 80°C (1) 		(3)

	<p>Differences</p> <ul style="list-style-type: none"> resistance of A decreases with temperature but resistance of B increases with temperature (1) for A, (largest slope/rate of change) is at lower temperature but for B, (largest slope/rate of change) is at higher temperature(s) (1) for B, resistance is constant below 50°C but for A resistance is roughly constant above 60°C (1) 	<p>accept (smallest slope/rate of change) for A is at higher temperature but (smallest slope/rate of change) for B is at lower temperature</p>	
--	---	--	--

Question number	Answer	Mark
3(c)(ii)	B	(1)

Question number	Answer	Mark
4(a)(i)	The earth wire discharges the aircraft to prevent sparking which could ignite the fuel/cause a fire	(1)

Question number	Answer	Additional guidance	Mark
4(a)(ii)	<p>An explanation that combines identification – understanding (1 mark) and reasoning/justification – understanding (1 mark):</p> <ul style="list-style-type: none"> friction between aircraft and air (1) causes electron transfer between aircraft and air (1) 	<p>accept idea of air rubbing against wings ignore 'charge' and 'static'</p> <p>do not allow (for second mark) idea of protons moving</p>	(2)

GCSE Physics 5PH2H/01 Mark Scheme – November 2012

Question Number	Answer	Acceptable answers	Mark
1(a)(i)	B		(1)

Question Number	Answer	Acceptable answers	Mark
1(a)(ii)	substitution (1) $V = 0.5 \times 12$ evaluation (1) $V = 6 \text{ (V)}$	Correct answer with no working shown gains two marks.	(2)

Question Number	Answer	Acceptable answers	Mark
1(a)(iii)	<ul style="list-style-type: none"> • P / ammeter reading would increase. (1) • Q / voltmeter reading would increase (1) 	They(both) would increase for two marks	(2)

Question Number	Answer	Acceptable answers	Mark
1(a)(iv)	(current/it) would decrease (1)	smaller/lower/reduce/less Ignore slowing down	(1)

Question Number	Answer	Acceptable answers	Mark								
1(b)	<table border="1" style="width: 100%; text-align: center;"> <tr> <td style="width: 50%;">component symbol</td> <td style="width: 50%;">graph</td> </tr> <tr> <td></td> <td></td> </tr> <tr> <td></td> <td></td> </tr> <tr> <td></td> <td></td> </tr> </table>	component symbol	graph							All three lines correct for 2 marks One or two lines correct for 1 mark More than one line against any box cannot score more than 1 mark in total.	(2)
component symbol	graph										

Question Number	Answer	Acceptable answers	Mark
3 (a) (i)	Correctly plotted point (1)	+/- ½ a small square	(1)

Question Number	Answer	Acceptable answers	Mark
3 (a)(ii)	Smooth line through most (at least 5) crosses / points (1)	Do not accept clearly dot-to-dot or excessive tramlining Ignore any part of line after 45	(1)

Question Number	Answer	Acceptable answers	Mark
3 (a) (iii)	Substitution: (1) $12 = 0.047 \times R$ Transposition: (1) $R = 12/0.047$ Evaluation: (1) $R = 260$	transposition and substitution in either order substitution mark can be scored when incorrectly transposed word/symbol equation is given 255.3, 255 give full marks for correct answer no working power of 10 errors with no working score max 1 mark	(3)

Question Number	Answer	Acceptable answers	Mark
3 (a) (iv)	An explanation linking <ul style="list-style-type: none"> • current increases with temperature (1) with <ul style="list-style-type: none"> • (so) resistance decreases(1) or <ul style="list-style-type: none"> • the voltage is constant (1) with • (so) resistance decreases (with temperature increase)(1) 	(for this first MP) ignore faster/slower (charge/current) ignore references to heat, current flows more can score both marks by quoting two suitable pairs of values from graph For full marks, there must be a reference to change of either I or R with temperature	(2)

Question Number	Answer	Acceptable answers	Mark
3 (b)(i)	<p>An explanation linking</p> <ul style="list-style-type: none"> • {electrons / negative charges} (1) • collide with {ions/lattice/electrons} (1) 	<p>atoms / nuclei</p> <p>allow for 1 mark, electrical energy transferred to {thermal/heat} energy if no other scored</p>	(2)

Question Number	Answer	Acceptable answers	Mark
3 (b) (ii)	<p>A suggestion including</p> <p>energy transfer in {the thermistor/ any component part of the electrical circuit} causes a rise in temperature of thermistor (above surroundings)(1)</p>	<p>thermistor/resistor {gets hot/is heated}</p>	(1)

Question Number	Answer	Acceptable answers	Mark
6 (a)(i)	B		(1)

Question Number	Answer	Acceptable answers	Mark
6 (a)(ii)	substitution $V = 0.039 \times 185$ (1) evaluation 7.215 (which is about 7.2) (V) (1)	Substitution $7.2 = I \times 185$ (1) transposition $I = 7.2 \div 185$ (1)	(2)

Question Number	Answer	Acceptable answers	Mark
6 (a)(iii)	C (same as)		(1)

Question Number	Answer	Acceptable answers	Mark
6(a)(iv)	An explanation to include The resistance (of the LDR) changes Greater resistance when in the dark	LDR has less resistance in the light	(2)

Question Number		Indicative Content	Mark
QWC	*6(b)	<p>An explanation linking some of the following.</p> <ul style="list-style-type: none"> • less current is used at night-time • Resistance (of LDR or circuit) would increase with less ambient light • Higher resistance will allow less current (in the circuit) (ORA) • Less current in circuit means less energy from the battery • Less power required in the dark ORA for light conditions • Less current means less energy transferred (per second) • Total energy transferred is less during night time (than it would otherwise have been) due to the higher resistance of the LDR 	(6)
Level	0	No rewardable content	
1	1 - 2	<ul style="list-style-type: none"> • A limited explanation linking the light level to EITHER resistance OR current. eg. It increases the resistance in the dark. • the answer communicates ideas using simple language and uses limited scientific terminology • spelling, punctuation and grammar are used with limited accuracy 	
2	3 - 4	<ul style="list-style-type: none"> • A simple explanation linking the light level to TWO of resistance, current, energy. eg. At night-time its resistance would increase. This would reduce the current from the battery • the answer communicates ideas showing some evidence of clarity and organisation and uses scientific terminology appropriately • spelling, punctuation and grammar are used with some accuracy 	
3	5 - 6	<ul style="list-style-type: none"> • A detailed explanation linking the light level to resistance AND current, AND energy. e.g. At night-time the resistance would be more. This would reduce the current and mean that the battery will not have to supply as much energy. • the answer communicates ideas clearly and coherently uses a range of scientific terminology accurately • spelling, punctuation and grammar are used with few errors 	

Total for Question 6 = 12 marks